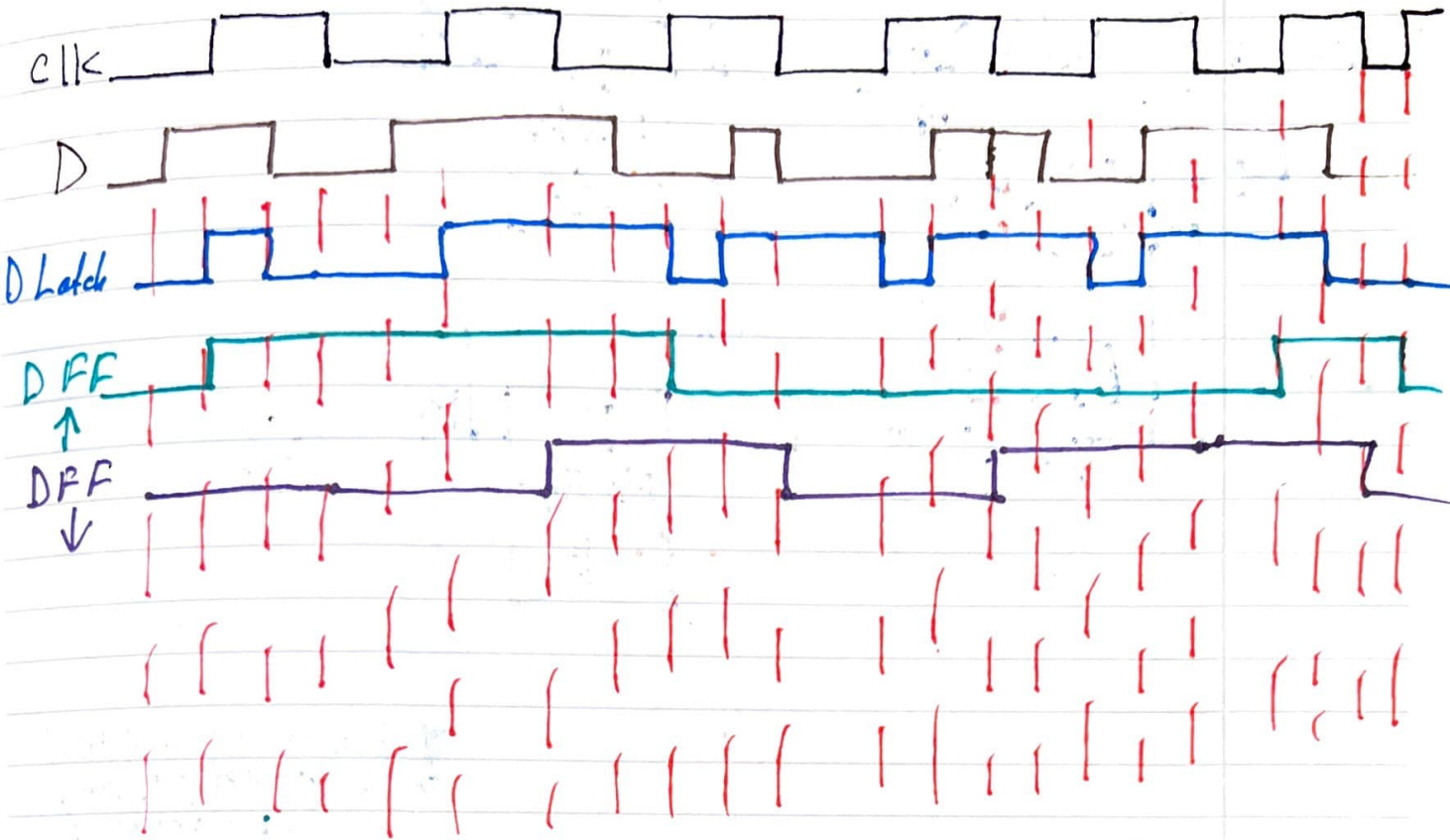


Homework 6

1) Waveforms for D Latch, DFF (↑), DFF (↓)




4. A sequential circuit with two D Flip Flops, A and B, two inputs x and y and one output z, is specified by the following next-state and output equations

$$A(t+1) = \overset{=0}{x'} \overset{=1}{y} + \overset{=1}{x} \overset{=1}{A}$$

$$B(t+1) = \overset{=0}{x'} \overset{=1}{B} + \overset{=1}{x} \overset{=1}{A}$$

$$z = B$$

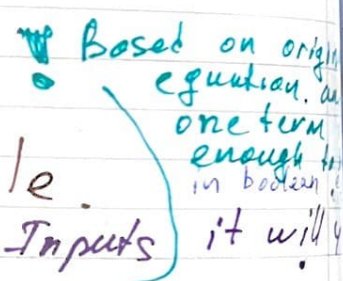


1

$$A(t+1) = D$$

4 steps / 3 steps / 2 steps / 1 step


[illegible]

c) State Diagram.

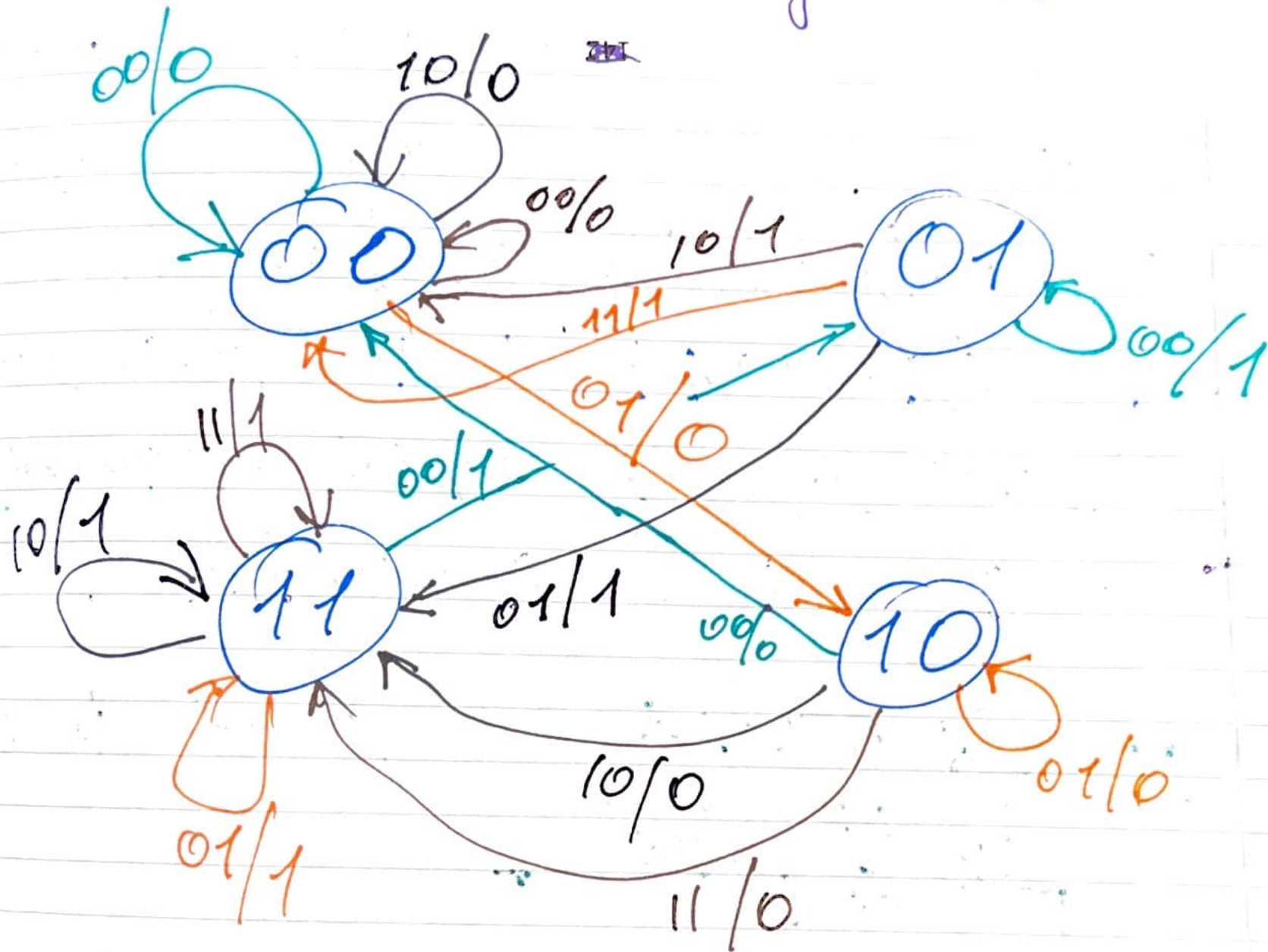

5. Sequential circuit has two JK FF A and B and one ~~one~~ input x. The circuit is described by the following FF input equation: $J_A = x, K_A = B, J_B = x, K_B = A'$

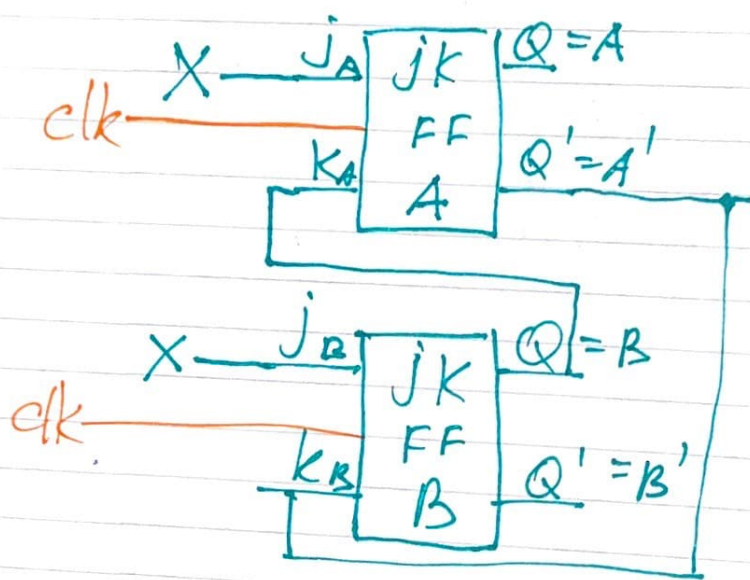a) Derive state equation $A(t+1)$ and $B(t+1)$ by substituting the input equations for the j and k variables.



$$A(t+1) = J_A = x$$

$$B(t+1) = J_B = x$$

Characteristic of JK FF $Q(t+1) = JQ' + K'Q$

now we have to substitute that expression

$$Q_A(t+1) = J_A Q' + K_A' Q = J_A \cdot A' + K_A' \cdot A = x \cdot A' + B \cdot A$$

expression for A JK FF


$$Q_B(t+1) = J_B Q' + K_B' Q = x \cdot B + A \cdot B$$

expression for B JK FF


b) List the stable for the sequential circuit

	Present State	Input	Next State	Output
	$A(t) \quad B(t)$	X	$A(t+1) \quad B(t+1)$	Y
00 S_0	0 0	0	0 0	0
	0 0	1	1 0	0
01 S_1	0 1	0	0 1	0
	0 1	1	1 1	1
10 S_2	1 0	0	1 0	0
	1 0	1	1 1	0
11 S_3	1 1	0	0 0	0
	1 1	1	0 1	1

c) Draw the state diagram of circuit

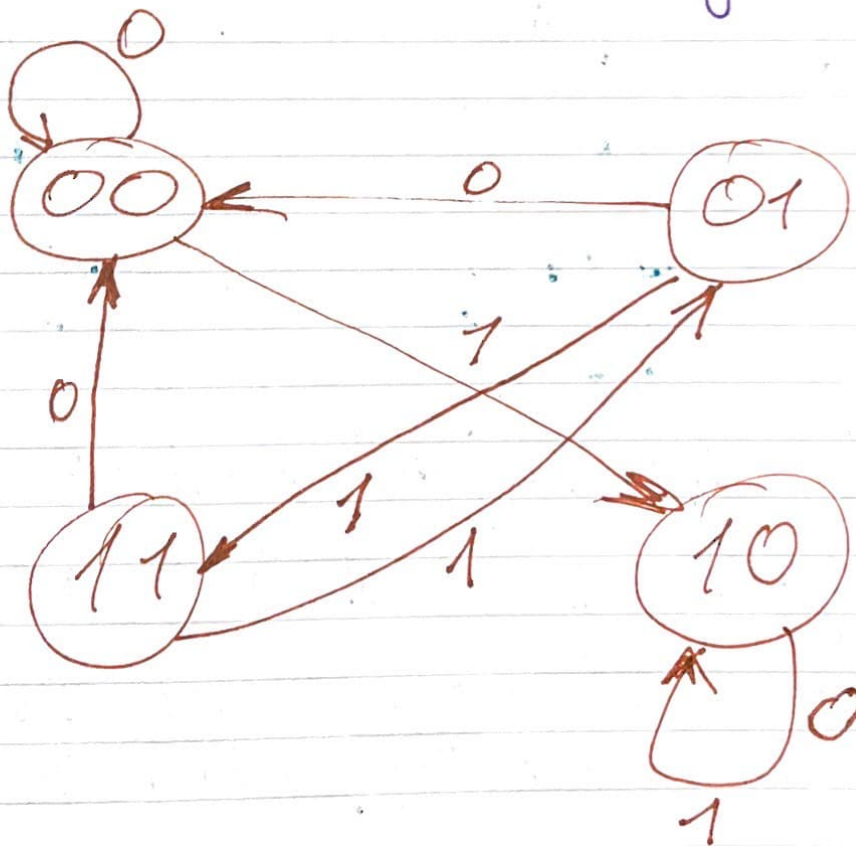

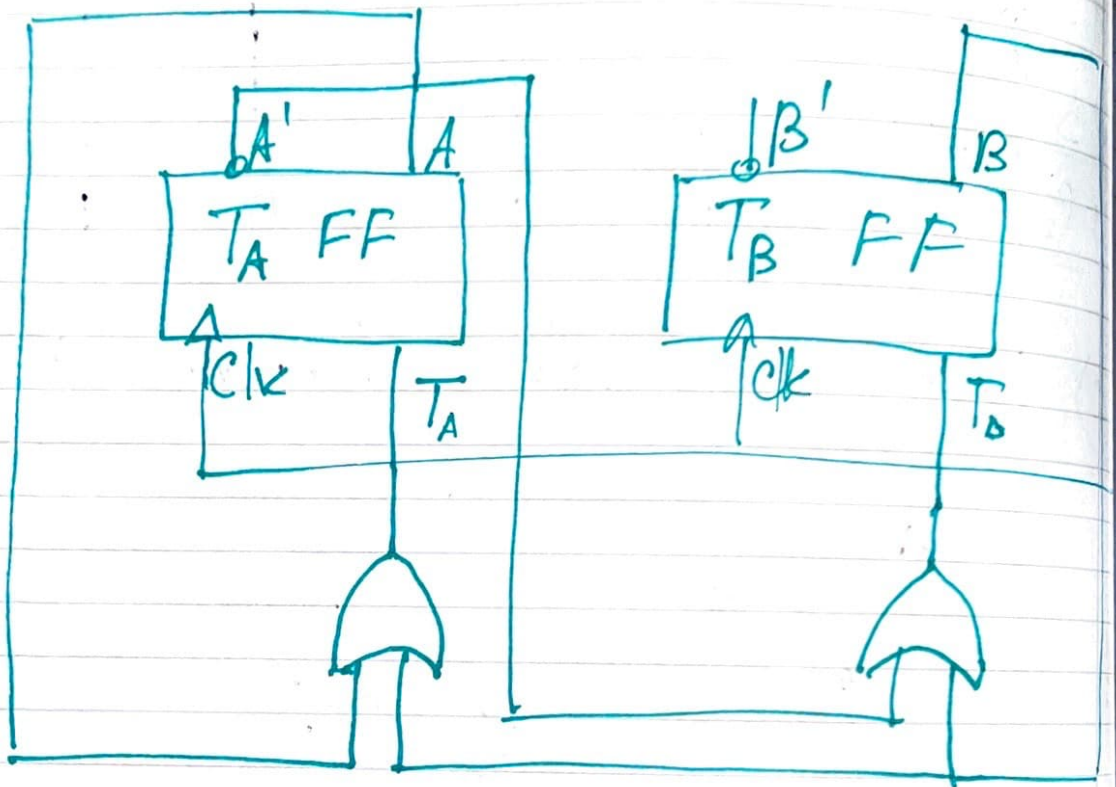6. Derive the state table and the state diagram of the sequential circuit shown in the following figure. Explain the function of the circuit.





$$A(t+1) = T_A = A(t) + B(t) = A + B$$

$$B(t+1) = T_B = B(t) + A'(t) = B + A'$$

Inputs		Present State		Inputs		Next State	State
T_A	T_B	$A(t)$	$B(t)$	T_A	T_B	$A(t+1)$	$B(t+1)$
		0	0	0	1	0	1
		0	1	1	1	1	0
		1	0	1	0	0	0
		1	1	1	1	0	0

- First we have to find inputs T_A, T_B values from equation base 4 combinations.
- Now we have everything to find Next State.

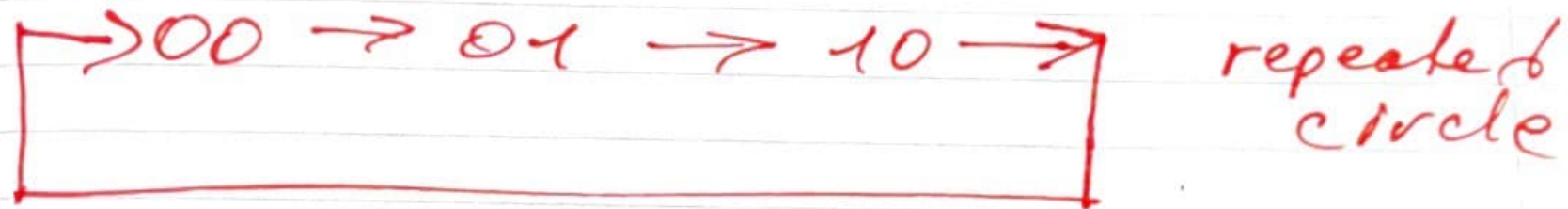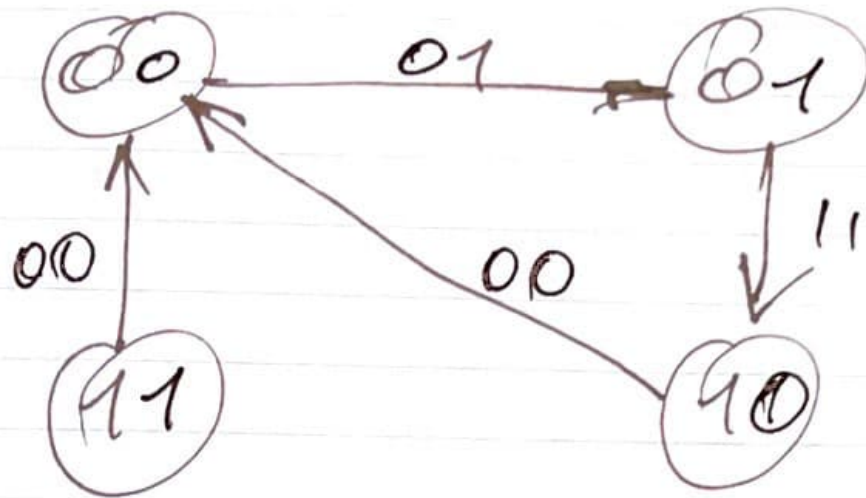Based on characteristic of TFF
 $Q(t+1) = T \oplus Q$ we find Next State



This circuit is a counter
with repeated sequence of 00, 01, 10.